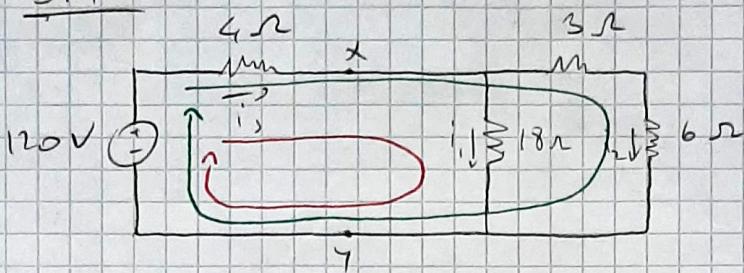


3.1



$$3\Omega + 6\Omega = 9\Omega \text{ (serial connected)}$$

$$\frac{1}{9} + \frac{1}{18} = \frac{1}{6} \Rightarrow 6\Omega \text{ (parallel connected)}$$

$$R_T = 6\Omega + 4\Omega = 10\Omega \text{ (serial connected)}$$

$$V = I \cdot R_T \Rightarrow 120 = I \cdot 10 \Rightarrow I = 12A$$

$$i_1 = 12A$$

a) Current entering the junction α is same as the current leaving junction α and the current is 12 A.

Current entering the junction γ is same as the current leaving junction γ and the current is 11 A.

b) According to KVL sum of voltages in any closed loop should be equal to zero.

First loop (red one)

$$4 \cdot 12 - i_{1,18} - 120 = 0 \Rightarrow i_{1,18} = 72 \Rightarrow i_1 = 4A$$


Second loop (green one)

$$4 \cdot 12 + i_{2,9} - 120 = 0 \Rightarrow i_{2,9} = 72 \Rightarrow i_2 = 8A$$

According to KCL $i_1 + i_2 + i_3 = 12$. It checks.

So KVL is correct for any closed loop

3.2

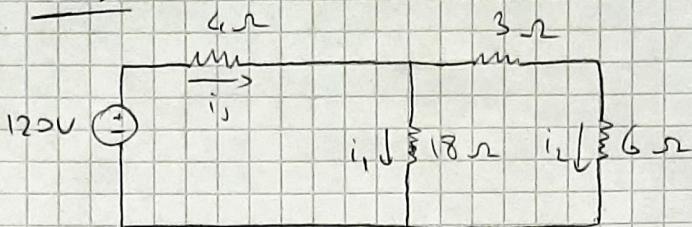

$$3\Omega + 6\Omega = 9\Omega \text{ (series connected)}$$

$$\frac{1}{3} + \frac{1}{18} = \frac{1}{6} \Rightarrow 6\Omega \text{ (parallel connected)}$$

$$R_T = 4\Omega + 6\Omega = 10\Omega \text{ (series connected)}$$

$$V = i_1 \cdot R_T \Rightarrow 120 = i_1 \cdot 10 \Rightarrow i_1 = 12A$$

$$i_1 \cdot 12 + i_1 \cdot 18 - 120 = 0 \Rightarrow i_1 \cdot 18 = 72 \Rightarrow i_1 = 4A \quad (\text{LVC})$$

$$(i_1 \cdot 12 + i_2 \cdot 9) - 120 = 0 \Rightarrow i_2 \cdot 9 = 72 \Rightarrow i_2 = 8A \quad (\text{LVC})$$

a) For 4Ω resistor

$$\rho = i^2 \cdot R \Rightarrow \rho = 12^2 \cdot 4 = 576 \mu$$

For 3Ω resistor

$$\rho = i^2 \cdot R \Rightarrow \rho = 8^2 \cdot 3 = 192 \mu$$

For 6Ω resistor

$$\rho = i^2 \cdot R \Rightarrow \rho = 4^2 \cdot 6 = 384 \mu$$

for 18Ω resistor

$$\rho = i^2 \cdot R \Rightarrow \rho = 12^2 \cdot 18 = 288 \mu$$





b) $\rho = V \cdot i \Rightarrow \rho = 120 \cdot 12 = 1440 \mu$

c) The power delivered should be equal to power dissipated.

$$1440 = 576 + 192 + 384 + 288 \checkmark \quad (\text{It checks.})$$





3.3

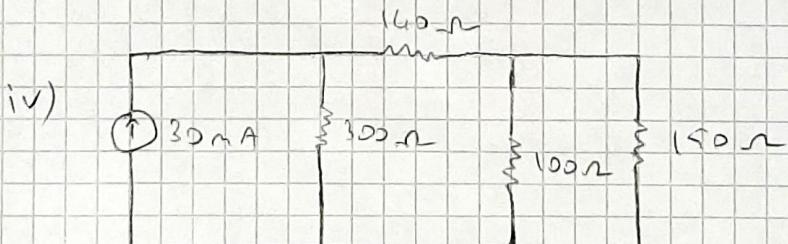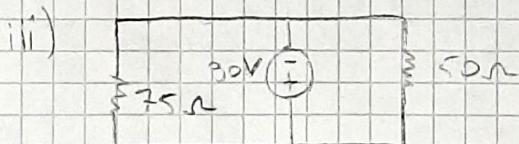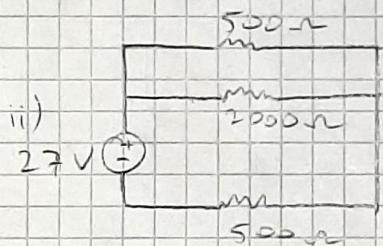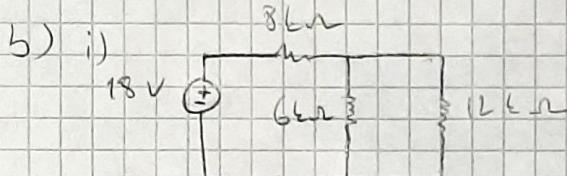- a) i) In P3.3 (a) circuit 56Ω and 76Ω resistors are connected in series.
- ii) In P3.3 (b) circuit 800Ω - 1000Ω and 800Ω - 200Ω are connected in series.
- iii) In P3.3 (c) circuit 35Ω - 15Ω - 25Ω and 10Ω - 40Ω are connected in series.
- iv) In P3.3 (d) circuit 50Ω - 90Ω and 80Ω - 70Ω are connected in series.



3.4

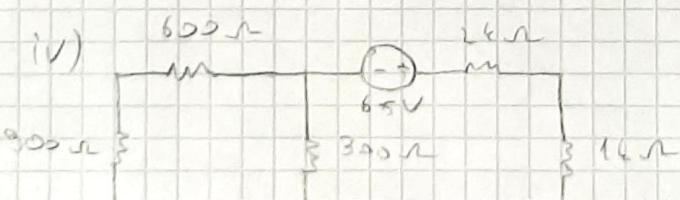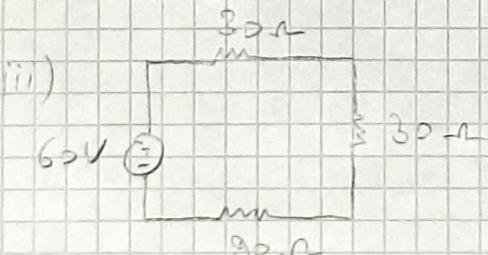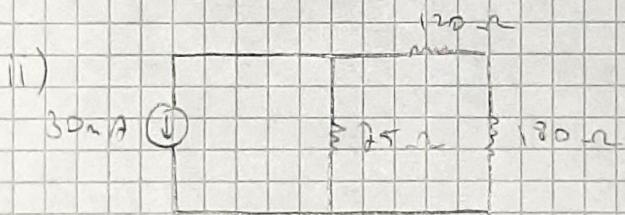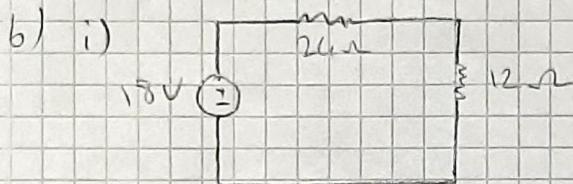- a) i) In P3.4.(a) circuit $36\Omega - 18\Omega$ are connected in parallel.
- ii) In P3.4.(b) circuit $210\Omega - 280\Omega$ and $200\Omega - 170\Omega - 180\Omega$ and 280Ω are connected in parallel.
- iii) In P3.4.(c) circuit $50\Omega - 25\Omega$ and $100k\Omega - 150k\Omega - 60k\Omega$ are connected in parallel.
- iv) In P3.4.(d) circuit $250\Omega - 500\Omega - 600\Omega$ and 500Ω , $1.5k\Omega - 3k\Omega$ are connected in parallel.



3.5

a) i) $5 + 7 = 12 \Omega$

$$\frac{1}{12} + \frac{1}{6} = \frac{1}{4} \Rightarrow 4 \Omega$$

$$R_T = 8 + 4 = 12 \Omega$$

ii) $800 + 1200 = 2000 \Omega$

$$\frac{1}{800} + \frac{1}{1200} = \frac{1}{400} \Rightarrow 400 \Omega$$

$$300 + 700 = 1000 \Omega$$

$$R_T = 500 + 600 = 900 \Omega$$

iii) $15 + 25 + 35 = 75 \Omega$

$$10 + 60 = 50 \Omega$$

$$\frac{1}{R_T} = \frac{1}{75} + \frac{1}{50} = \frac{1}{30}$$

$$R_T = 30 \Omega$$

iv) $80 + 70 = 150 \Omega$

$$\frac{1}{150} + \frac{1}{100} = \frac{1}{60} \Rightarrow 60 \Omega$$

$$50 + 90 + 60 = 200 \Omega$$

$$\frac{1}{R_T} = \frac{1}{200} + \frac{1}{320} = \frac{1}{120}$$

$$R_T = 120 \Omega$$

3.5

b) i) $V = I \cdot R \Rightarrow 18 = I \cdot 12 \quad I = 1,5 A$

$$\rho = V \cdot I \Rightarrow 18 \cdot 1,5 = 27 \text{ W} \cancel{\parallel}$$

ii) $V = I \cdot R \Rightarrow 27 = I \cdot 300 \quad I = 0,03 A$

$$\rho = V \cdot I \Rightarrow 27 \cdot 0,03 = 0,81 \text{ W} \parallel$$

iii) $V = I \cdot R \Rightarrow 90 = I \cdot 30 \quad I = 3 A$

$$\rho = V \cdot I \Rightarrow 90 \cdot 3 = 270 \text{ W} \cancel{\parallel}$$

iv) $V = I \cdot R \Rightarrow 0,03 = I \cdot 120 \quad I = 0,00025 A$

$$\rho = V \cdot I \Rightarrow 0,03 \cdot 0,00025 = 7,5 \cdot 10^{-6} \text{ W} \parallel$$

3.8

a) $\frac{1}{60} + \frac{1}{90} = \frac{1}{36} \Rightarrow 36 \text{ m}$

$$R_{\text{obj}} = 21 + 36 + 12 = 72 \text{ m}$$

b) $6 + 2 + 4 = 12 \text{ m}$

$$\frac{1}{12} + \frac{1}{8} = \frac{1}{6,8} \Rightarrow 6,8 \text{ m}$$

$$R_{\text{obj}} = 6,8 + 5,2 = 10 \text{ m}$$


c) $\frac{1}{1200} + \frac{1}{720} = \frac{1}{450} \Rightarrow 450 \text{ m}$

$$320 + 180 = 800 \text{ m}$$

$$\frac{1}{450} + \frac{1}{500} = \frac{1}{280}$$

$$R_{\text{obj}} = 280 \text{ m}$$

3.13

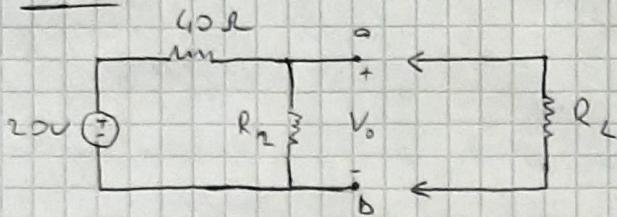

$$V_o = V_s \frac{R_2}{R_2 + 40}$$

$$4 = 20 \cdot \frac{R_2}{R_2 + 40} \Rightarrow \frac{R_2}{R_2 + 40} = \frac{1}{5}$$

$$R_2 = 10 \Omega$$

$$V = I \cdot R \Rightarrow 20 = 50 \cdot I \quad I = 0,4 \text{ A}$$


$$R_2 \cdot i_1 = 3V \Rightarrow 10 \cdot i_1 = 3V \quad i_1 = 0,3 \text{ A}$$

$$40 \cdot i_7 = 17V \quad i_7 = 17/40 \text{ A}$$

$$i_2 = 17/40 - 3/10 = 0,125 \text{ A}$$

$$R_L \cdot 0,125 = 3V \Rightarrow R_L = 24 \Omega$$

3.17

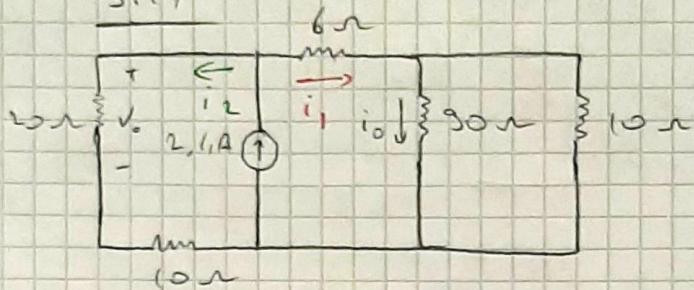

$$a) \frac{1}{90} + \frac{1}{10} = \frac{1}{9} \Rightarrow 9 \text{ n} \quad 9 + 6 = 15 \text{ n}$$

$$R_0 + 10 = 30 \text{ n}$$

$$i_1 = 1,6 \text{ A}$$

$$i_0 = 0,16 \text{ A} //$$

$$i_2 = 0,3 \text{ A}$$

$$V_0 = 0,8 \cdot 20 = 16 \text{ V}_{\parallel}$$


$$b) P = i^2 \cdot R \Rightarrow (1,6)^2 \cdot 6 = 15,36 \text{ W}_{\parallel}$$

$$c) \frac{1}{R_T} = \frac{1}{30} + \frac{1}{15} = \frac{1}{10} \Rightarrow R_T = 10 \text{ n}$$

$$V = I \cdot R \Rightarrow V = 10 \cdot 2,6 = 26 \text{ V}_{\parallel}$$

$$P = V \cdot I \Rightarrow P = 26 \cdot 2,6 = 67,6 \text{ W}_{\parallel}$$

3.18

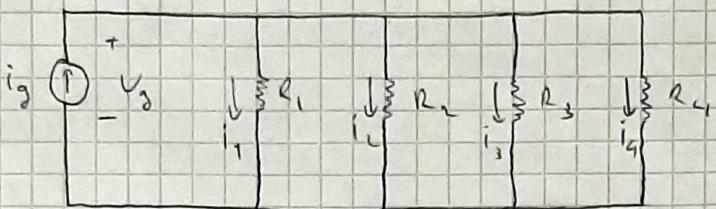

Criterias:

$$i_g = 50 \text{ mA}, \quad V_g = 25 \text{ V}, \quad i_1 = 0.6 i_2, \quad i_3 = 2 i_2$$

$$\text{and } i_4 = 4 i_1$$

$$i_2 = 5/3 i_1$$

$$10 i_1 = 50 \text{ mA}$$

$$i_1 = 5 \text{ mA}$$

$$i_2 = 25/3 \text{ mA}$$

$$i_1 = 4 i_3$$

$$i_3 = 50/3 \text{ mA}$$

$$i_4 = 20 \text{ mA}$$

$$25 = 0.005 \cdot R_1$$

$$25 = \frac{1}{R_1} \cdot R_2$$

$$R_1 = 5 \text{ k}\Omega$$

$$R_2 = 3 \text{ k}\Omega$$


$$25 = \frac{1}{60} \cdot R_3$$

$$25 = 0.02 \cdot R_4$$

$$R_3 = 1.5 \text{ k}\Omega$$

$$R_4 = 1.25 \text{ k}\Omega$$

3.19

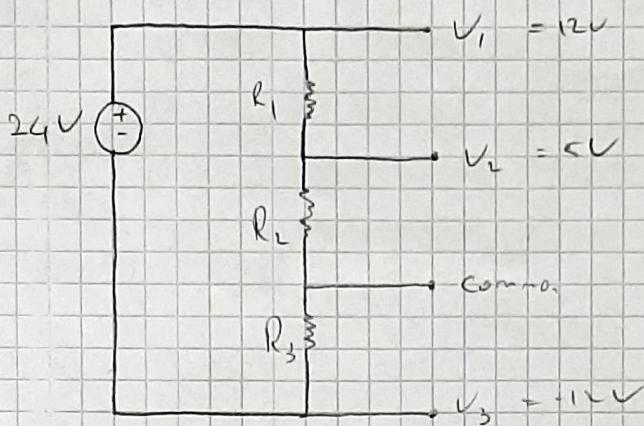

$$I = \frac{80}{24} = 10/3 A$$


$$R_1 \cdot \frac{10}{3} = 12 - 5 \Rightarrow R_1 = 2,1 \Omega$$

$$R_2 \cdot \frac{10}{3} = 5 - 0 \Rightarrow R_2 = 1,5 \Omega$$

$$R_3 \cdot \frac{10}{3} = 0 - (-11) \Rightarrow 3,6 \Omega$$

3.2

a)

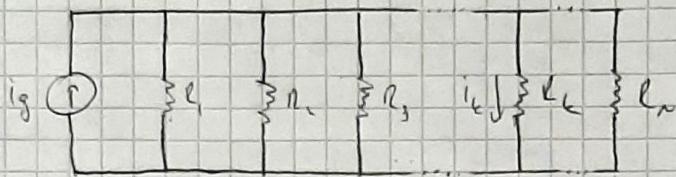

Show


$$i_L = \frac{i_g \cdot G_1}{G_1 + G_2 + G_3 + \dots + G_n}$$

$$G = \frac{1}{R} \Rightarrow G_1 + G_2 + G_3 + \dots + G_n = \frac{1}{R_T}$$

$$= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n} = \frac{1}{R_T}$$

$$i_L = i_g \cdot \frac{1}{R_T} \quad \text{This is valid for parallel circuits}$$

b)

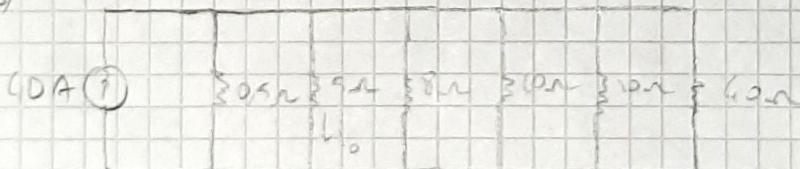


$$\frac{1}{R_7} = \frac{1}{(40)} + \frac{1}{5} + \frac{1}{8} + \frac{1}{10} + \frac{1}{15} + \frac{1}{40} = \frac{100}{600}$$

$$R_7 = 2.5 \Omega$$

$$i_B = 40 \cdot \frac{2}{25} = 3.2 A_{II}$$

3.28

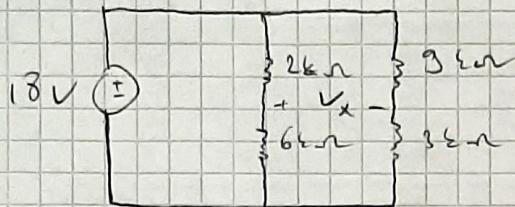

$$a) \frac{1}{R_1} = \frac{1}{8} + \frac{1}{12} = \frac{5}{24}, \quad R_{\text{eq}} = \frac{24}{5} \text{ ohms}$$

$$18 \cdot \frac{5}{24} = \frac{15}{4} \text{ A} = I$$

$$\frac{15}{4} \cdot \frac{3}{5} = \frac{3}{4}, \quad 4000 \cdot \frac{3}{4} = \frac{9}{2} \text{ V} \quad 18 - \frac{9}{2} = \frac{27}{2} \text{ V}$$

$$\frac{15}{4} \cdot \frac{2}{5} = \frac{1}{2} \cdot 9000 = \frac{27}{2} \text{ V} \quad 18 - \frac{27}{2} = \frac{5}{2} \text{ V}$$

$$V_x = \frac{23}{2} - \frac{5}{2} = \frac{18}{2} = 9 \text{ V}$$


$$b) R_1 = \frac{24}{5} \text{ ohms} \quad I = \frac{5U_1}{24000} \text{ A}$$

$$\frac{5U_1}{24000} \cdot 4000 \cdot \frac{3}{4} = \frac{15}{4} \quad U_3 - \frac{U_1}{4} = \frac{3U_1}{4}$$

$$\frac{5U_1}{24000} \cdot 8000 \cdot \frac{2}{4} = \frac{3U_1}{4} \quad U_3 - \frac{3U_1}{4} = \frac{U_1}{4}$$

$$U_x = \frac{3U_1}{4} - \frac{U_1}{4} = \frac{U_1}{2} \text{ V}$$

3.32

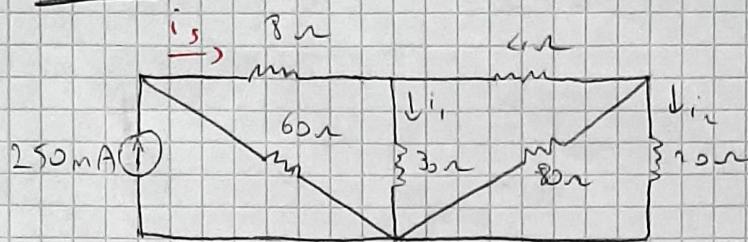

$$\frac{1}{8\Omega} + \frac{1}{6\Omega} = \frac{1}{16\Omega} \Rightarrow 16\Omega$$

$$16\Omega + 4\Omega = 20\Omega$$

$$\frac{1}{20\Omega} + \frac{1}{3\Omega} = \frac{1}{12\Omega} \Rightarrow 12\Omega$$

$$12\Omega + 8\Omega = 20\Omega$$


$$\frac{1}{20\Omega} + \frac{1}{6\Omega} + \frac{1}{15\Omega} = 15\Omega^{-1} = R_T$$

$$i_s = 250 \cdot \frac{15}{20} = 187,5 \text{ mA}$$

$$i_1 = 187,5 \cdot \frac{12}{30} = 75 \text{ mA}$$

$$i_2 = 187,5 \cdot \frac{16}{20} = 150 \text{ mA}$$

3.52

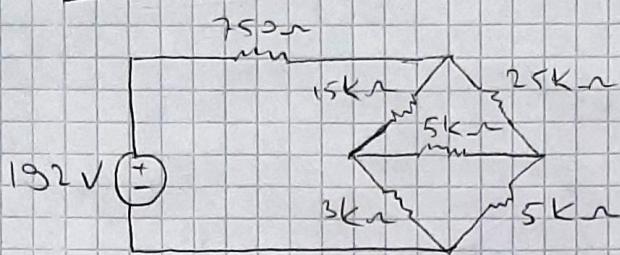

Current doesn't pass the middle $5\text{k}\Omega$ resistor

$$15+3 = 18 \quad 25+5 = 30$$

$$\frac{1}{18} + \frac{1}{30} = \frac{8}{90} \Rightarrow 11.25\text{k}\Omega$$


$$11.25 \rightarrow 0.75 = 12.5\text{k}\Omega$$

$$I = \frac{192}{12} = 16\text{mA}$$


$$16 \cdot \frac{11.25}{18} = 10\text{mA}$$

$$P = i^2 \cdot R \Rightarrow (0.01)^2 \cdot 3000 = 300\text{mW}$$

3.53

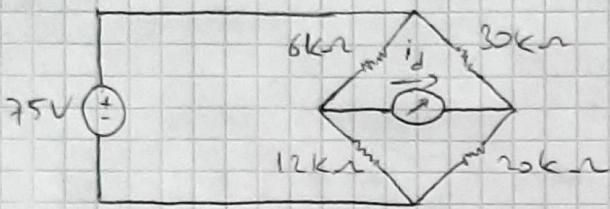

This can be converted to

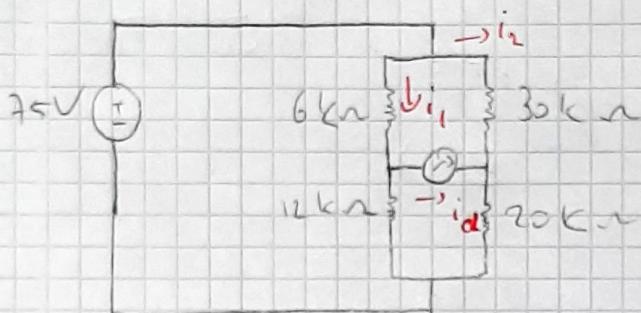

$$\frac{1}{6} + \frac{1}{30} = \frac{1}{5} \Rightarrow 5\text{k}\Omega$$

$$\frac{1}{20} + \frac{1}{12} = \frac{1}{7.5} \Rightarrow 7.5\text{k}\Omega$$

$$7.5 + 5 = 12.5\text{k}\Omega \quad I = 75 / 12.5 = 6\text{mA}$$


$$i_1 = 6 \cdot \frac{5}{6} = 5\text{mA} \quad i_d = x$$

$$i_2 = 6 \cdot \frac{5}{30} = 1\text{mA}$$

$$12.5(5-x) = 20(1+x) \Rightarrow 62.5 - 12.5x = 20x + 20$$

$$32x = 40$$



$$x = 1.25 \text{ mA}$$

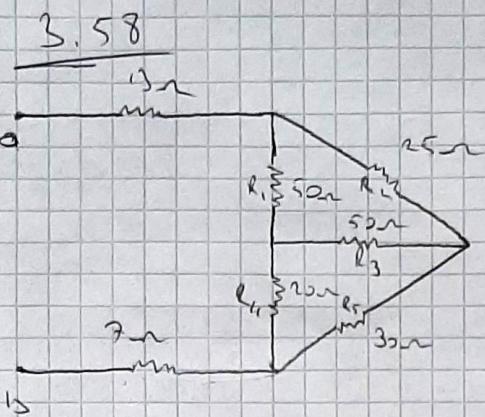

$$\text{a) } R_o = \frac{25,50 + 25,30 + 50,30}{25} = 140 \Omega$$

$$R_b = \frac{25,50 + 15,30 + 50,30}{50} = 70 \Omega$$
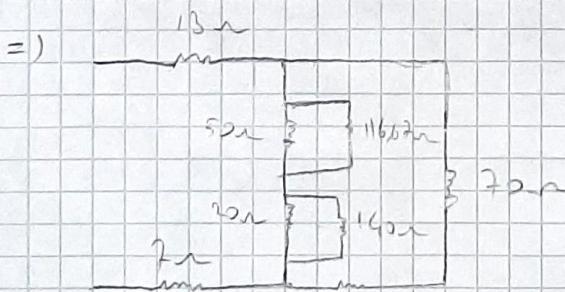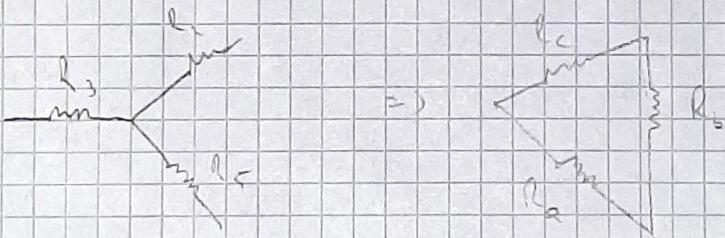
$$R_c = \frac{25,50 + 25,30 + 50,30}{30} = 116,67 \Omega$$



$$50 || 116,67 = 35 \Omega$$


$$20 || 16,67 = 17,5 \Omega$$

$$70 || 17,5 = 30 \Omega$$


$$30 + 13 + 7 = 50 \Omega = R_{ab}$$

3.58


b)

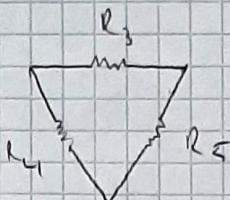

\Rightarrow

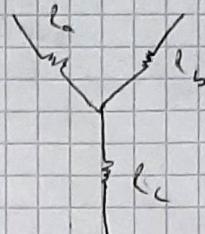
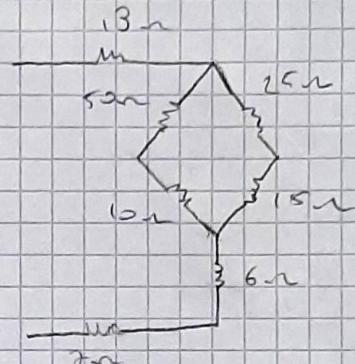
$$l_1 = \frac{50 \cdot 70}{100} = 35 \Omega$$



$$l_2 = \frac{50 \cdot 30}{100} = 15 \Omega$$

$$l_3 = \frac{70 \cdot 30}{100} = 21 \Omega$$

$$60 \parallel 40 = 24 \Omega$$

$$l_{0,1} = 24 + 6 + 13 + 7 = 50 \Omega //$$

c) $\Delta \rightarrow Y (R_1, R_2, R_3)$

$$l_1 = \frac{50 \cdot 25}{115} = 10 \Omega$$

$$40 \parallel 40 = 20 \Omega$$

$$l_2 = \frac{50 \cdot 15}{115} = 10 \Omega$$

$$l_{0,2} = 20 + 10 + 13 + 7 = 50 \Omega //$$

$$l_3 = \frac{50 \cdot 25}{115} = 10 \Omega$$

$Y \rightarrow \Delta (l_1, l_2, l_3)$

$$l_0 = \frac{1500}{70} = 21.4 \Omega$$

$$22.5 \parallel 25 = 22.5 \Omega // 15 \Omega$$

$$l_1 = \frac{4500}{50} = 90 \Omega$$


$$30 \parallel 30 = 22.5 \Omega$$

$$R_C = \frac{4500}{70} = 64.3 \Omega$$

$$90 \parallel 6.5 = 30 \Omega$$

$$l_{0,3} = 30 + 13 + 7 = 50 \Omega //$$

3.62

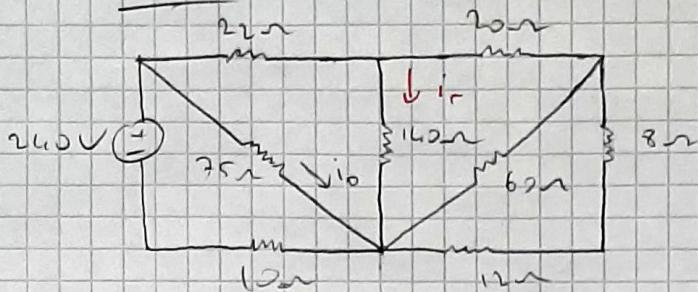

$$8 + 12 = 20 \Omega$$

$$20 \parallel 16\Omega = 15 \Omega$$

$$20 + 15 = 35 \Omega$$

$$16 \parallel 11 = 28 \Omega$$

$$28 + 22 = 50 \Omega$$

$$50 \parallel 75 = 30 \Omega$$

$$R_{eq} = 30 + 10 = 40 \Omega$$


$$I = 240 / 40 = 6 A$$

$$I_0 = 6 \cdot \frac{30}{75} = 2.4 A$$



$$I_F = 3.6 \cdot \frac{28}{40} = 2.52 A$$

$$P = I^2 \cdot R \Rightarrow (0.72)^2 \cdot 14 \Omega = 72.58 W //$$


3.67

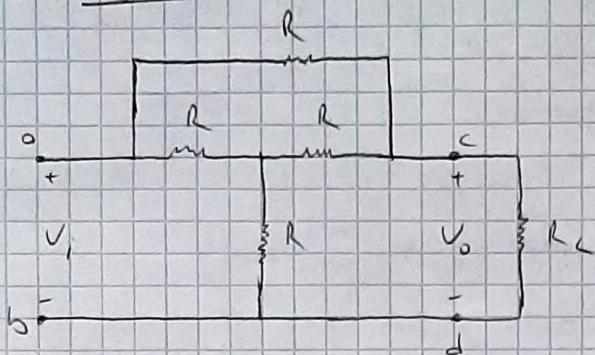

a)

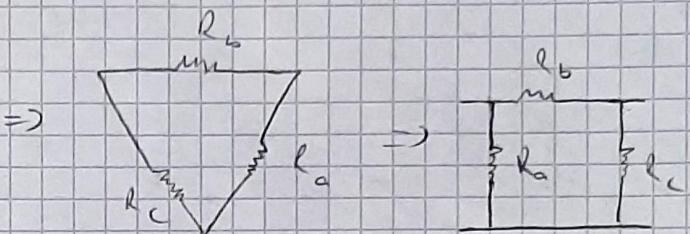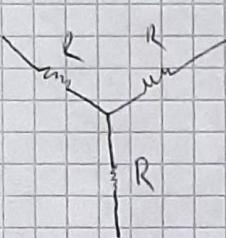

$$l_b = l_a = l_c = \frac{3R}{3} = R$$

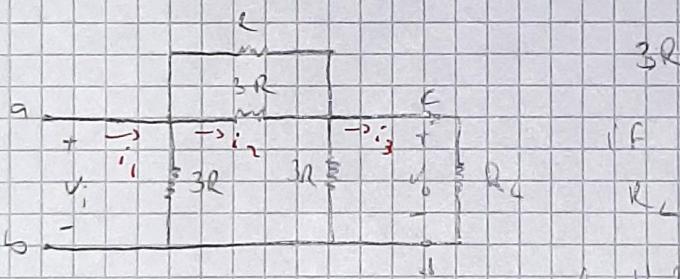

$$3R \parallel R = \frac{R}{4}$$

If we replace R with

$$R \parallel R_L = \frac{R_L}{2}$$

$$\frac{3R}{4} + \frac{3R}{4} = \frac{3R}{2}$$

$$\frac{3R}{2} \parallel 3R_L \Rightarrow R_L = R_{eq} \parallel$$

b) Let's assume that $i_1 = i$.

$$i_2 = i, \frac{R}{3R_L} = \frac{i_2}{3}$$


$$i_3 = \frac{2i}{3} \cdot \frac{\frac{3R_L}{i_1}}{R_L} = \frac{1}{2}$$

$$V_i = i \cdot l_b = i \cdot R_L$$

$$\frac{V_o}{V_i} = \frac{i \cdot R_L}{i \cdot R_L} = 0.5$$

$$V_o = \frac{1}{2} \cdot R_L$$

3.73

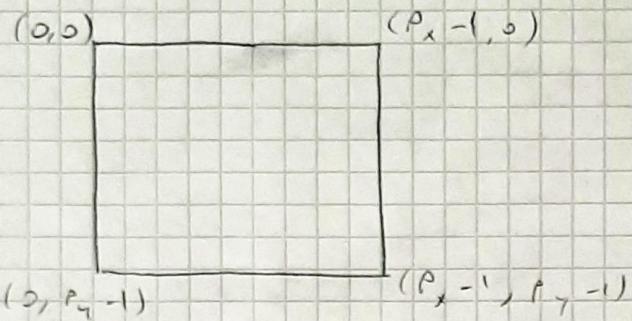

$$a) \alpha = \frac{V_x}{V_s} \quad \beta = \frac{V_y}{V_s}$$

$$V_s = 5V \quad \alpha = \frac{1}{5} = 0,2$$

$$V_x = 1V \quad \beta = \frac{3,75}{5} = 0,75,$$

$$V_y = 3,75V$$


$$b) x = (1 - \alpha) \cdot \rho_x$$

$$y = (1 - \beta) \cdot \rho_y$$

$$x = (1 - 0,2) \cdot 680 = 0,8 \cdot 680 = 544$$

$$y = (1 - 0,75) \cdot 800 = 0,25 \cdot 800 = 200$$

3.761

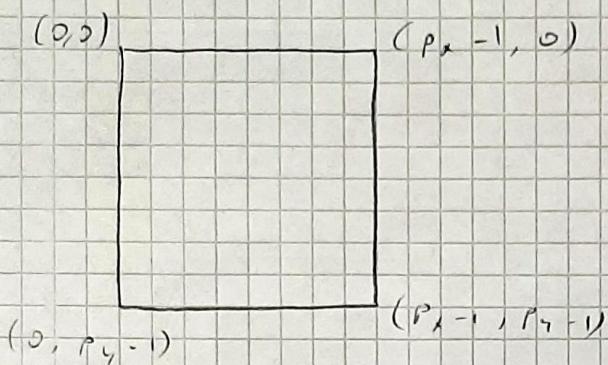

$$\frac{3}{13} \cancel{6} = (1 - \alpha) \cancel{6} \Rightarrow \alpha = 1/6$$

$$\frac{13}{16} = (1 - \beta) \cancel{16} \Rightarrow \beta = 13/16$$

$$\frac{1}{6} = \frac{V_x}{8} \Rightarrow V_x = 2V_f$$

$$\frac{13}{16} = \frac{V_y}{8} \Rightarrow V_y = 6.5V_f$$